


Control of VSC-HVDC for Multiterminal Operation

PhD Candidate: Temesgen Haileselassie

Supervisors: Prof. Kjetil Uhlen, Prof. Tore Undeland

Norwegian University of Science and Technology (NTNU)

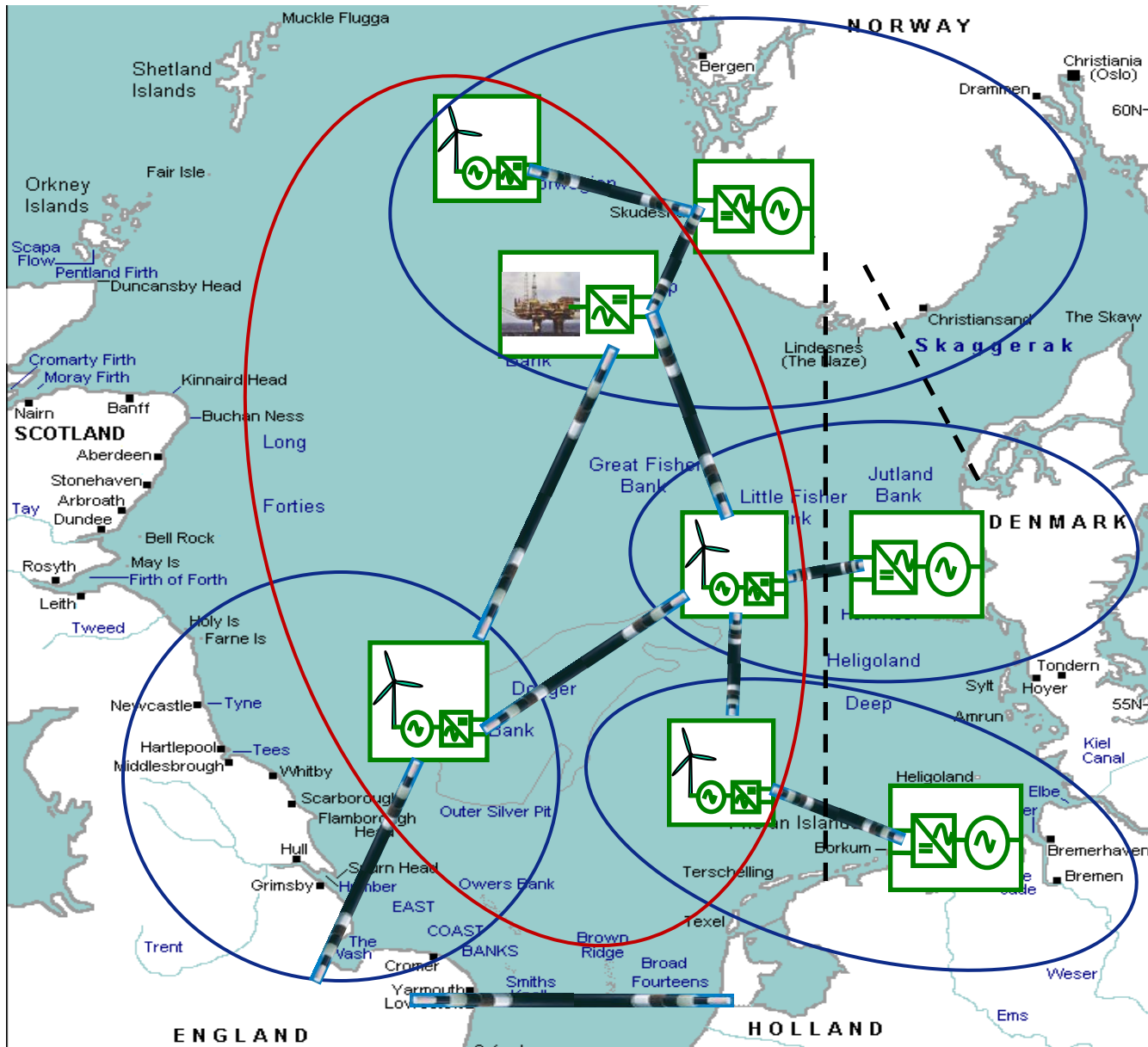Background: AC/DC Grid integration in the North Sea



Desired operational capabilities of MTDC

- Balancing of offshore wind power variation
- Tolerance to loss of a VSC-HVDC terminal (\approx load/generation loss)
- Frequency response enhancement of AC grids
- Market integrated operation
- AC and DC fault handling capabilities

Active and Passive AC grid Connections


Passive AC grid connection:

- AC voltage control at PCC
- no synchronization
- no control of current

Active AC grid connection:

- Grid synchronization
- control of current flow

Time-average VSC model

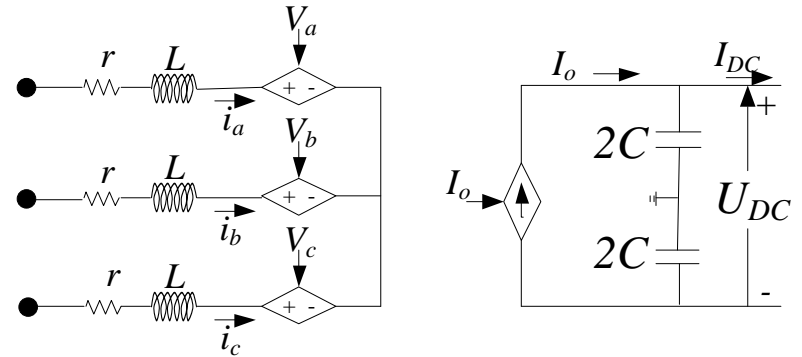


$$V_a = \frac{m_a U_{dc}}{2}, \quad V_b = \frac{m_b U_{dc}}{2}, \quad V_c = \frac{m_c U_{dc}}{2}$$

$$I_o = \frac{1}{2} (m_a i_a + m_b i_b + m_c i_c)$$

Control of VSC Connected to Passive AC Grid

AC voltage control at PCC, $|V|$

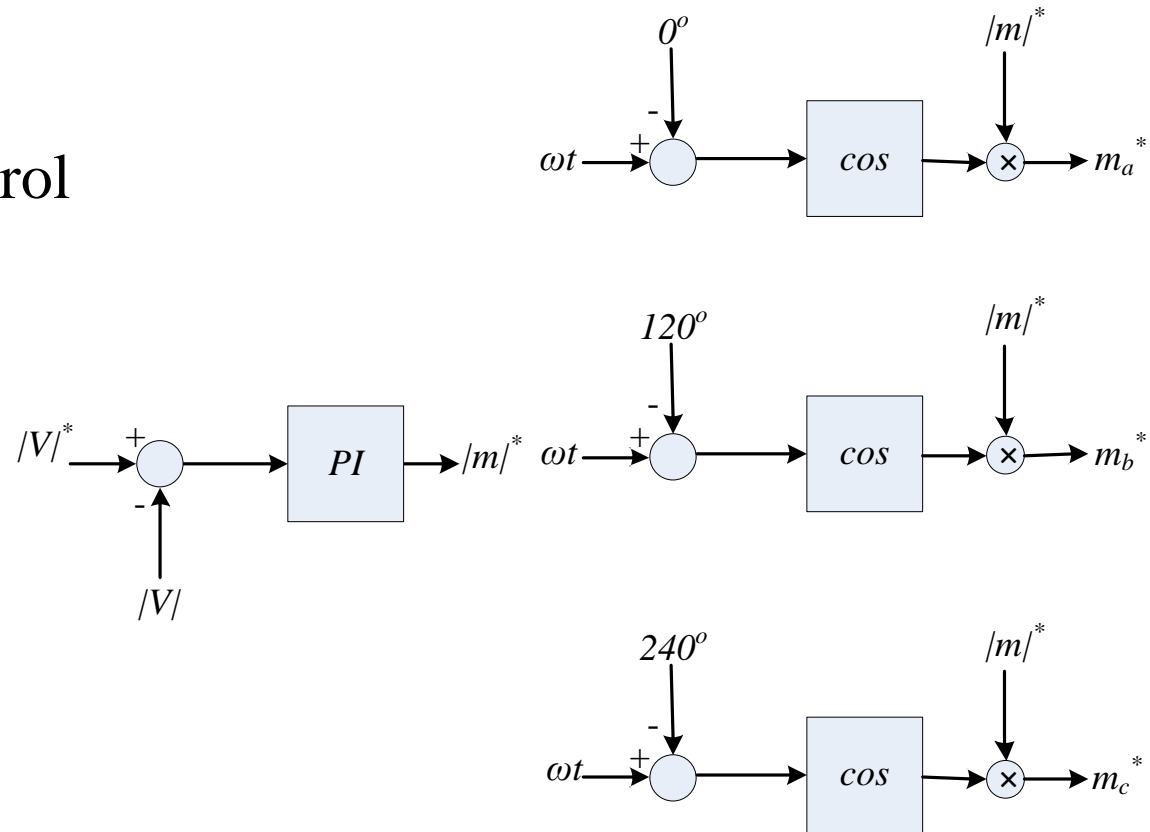


Control of VSC Connected to Active AC grid

Two options:

- *$|m|$, δ control*: uses phasor measurements
- *decoupled axes (dq) control* : uses instantaneous measurements


$|m|, \delta$ control

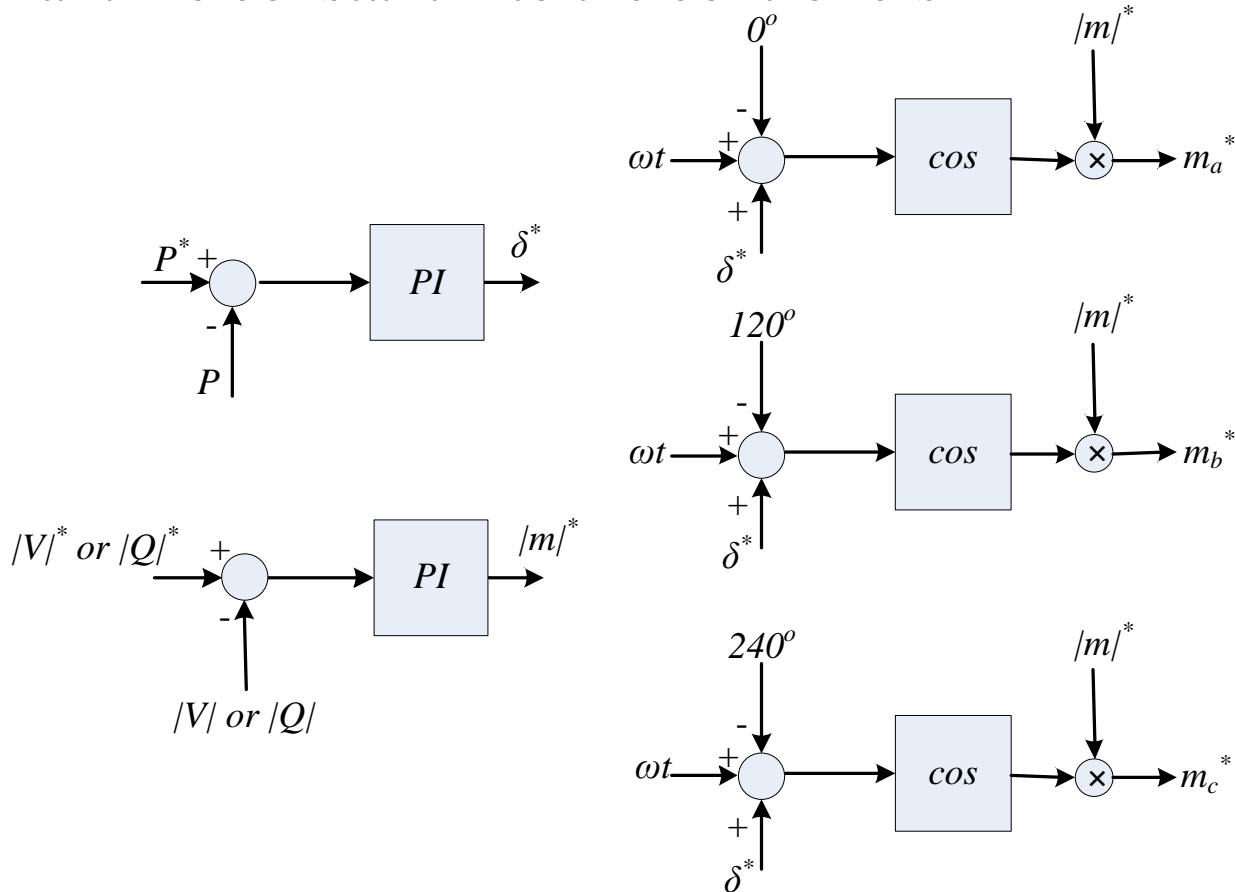- Suitable for modelling VSC control in phasor based electric power simulation tools (eg: DIgSILENT).
- Voltage and current phasor measurements introduce additional time constant into the controllers





Decoupled axes (dq) control


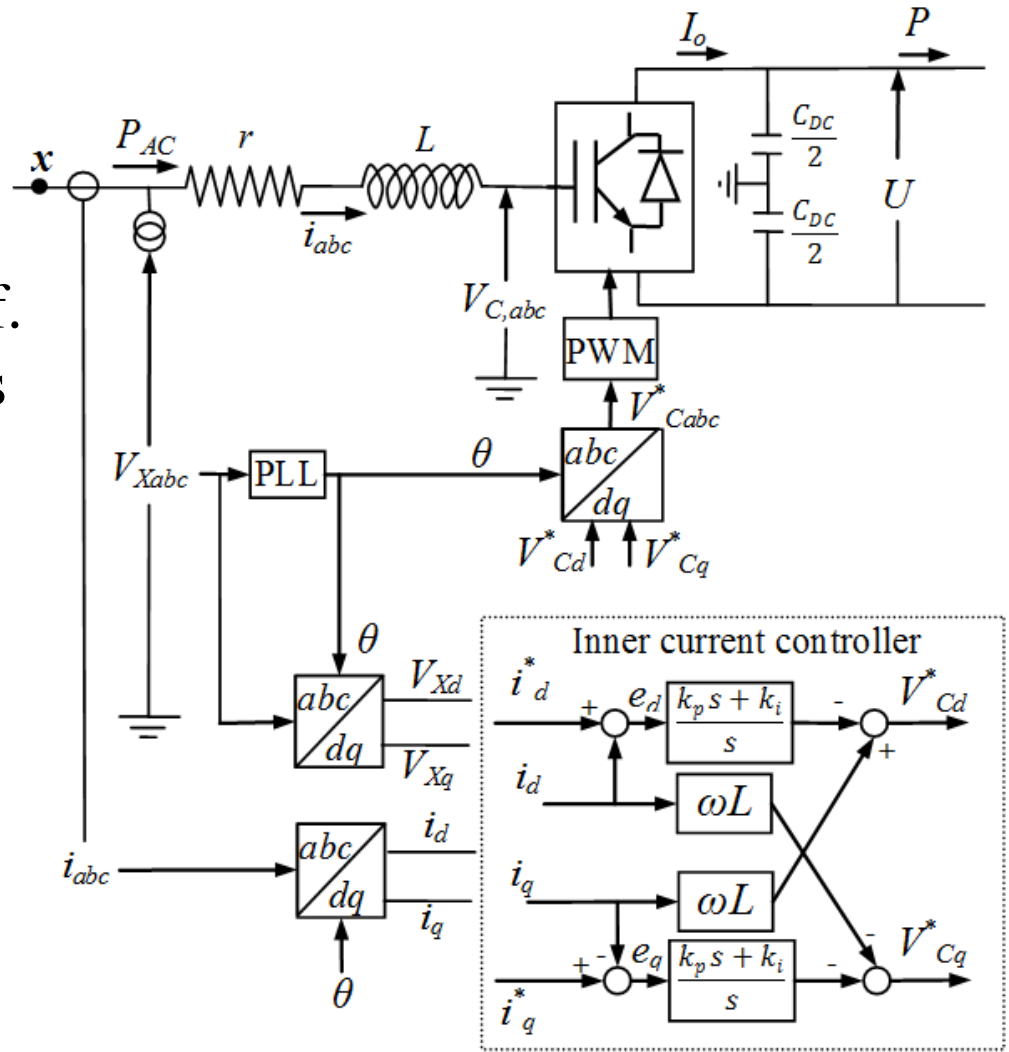
- Involves abc/dq transf.
- Fast control responses
- Practically used in VSC control
- Modelling is possible with electromagnetic transient softwares such as PSCAD





Outer Controllers

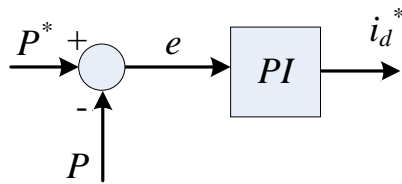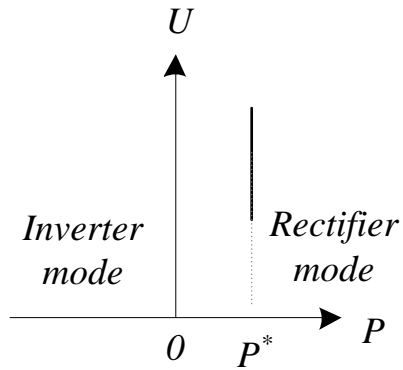

a. Fixed power control

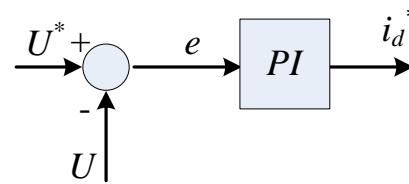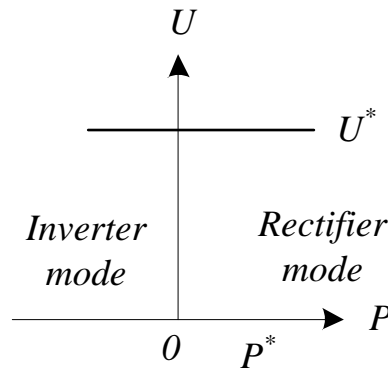


b. Fixed DC voltage control

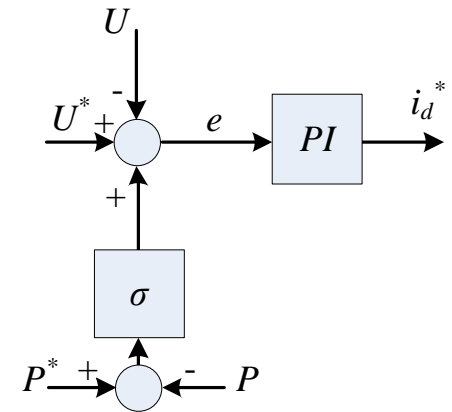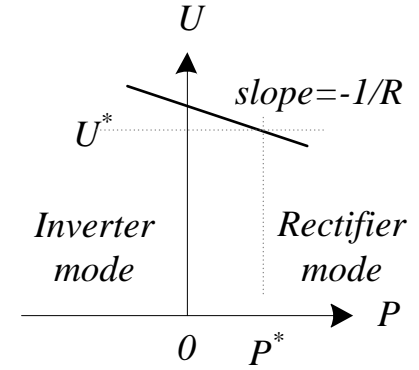

c. DC voltage droop controller





Two terminal VSC-HVDC Control

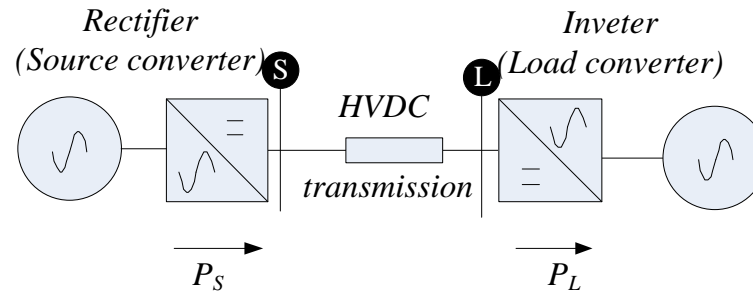


Control modes		Remarks
Rectifier	Inverter	
Fixed power	Fixed power	X (Not viable)
Fixed power	DC Droop	√ (With risk of DC overvoltage)
Fixed power	Fixed DC voltage	√ (With risk of DC overvoltage)
DC Droop	Fixed power	√ (Good, P control by Inv.)
DC Droop	DC Droop	√ (Good, P control by Both)
DC Droop	Fixed DC voltage	√ (OK, P control by Rect.)
Fixed DC voltage	Fixed power	√ (Good, P control by Inv.)
Fixed DC voltage	DC Droop	√ (Good, P control by Inv.)
Fixed DC voltage	Fixed DC voltage	X (Not viable)

DC Voltage Control Responses


(Primary & secondary DC voltage control)

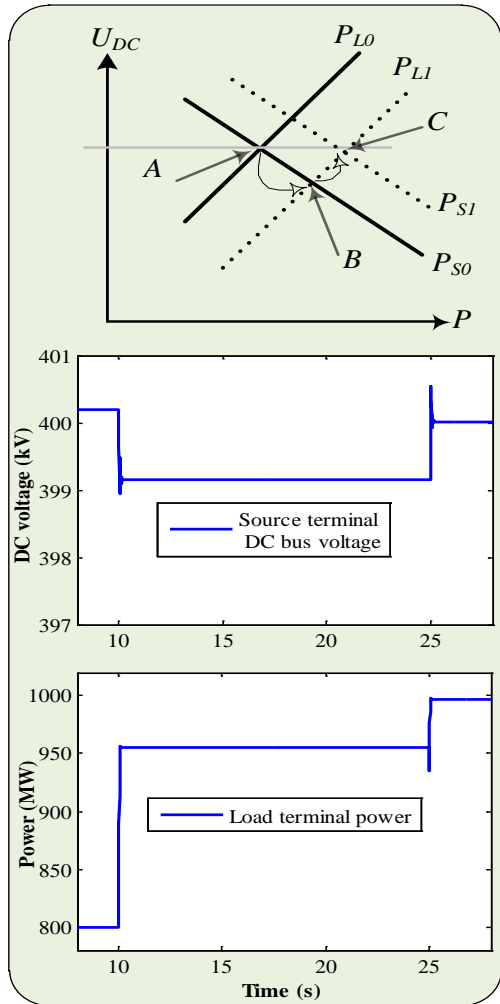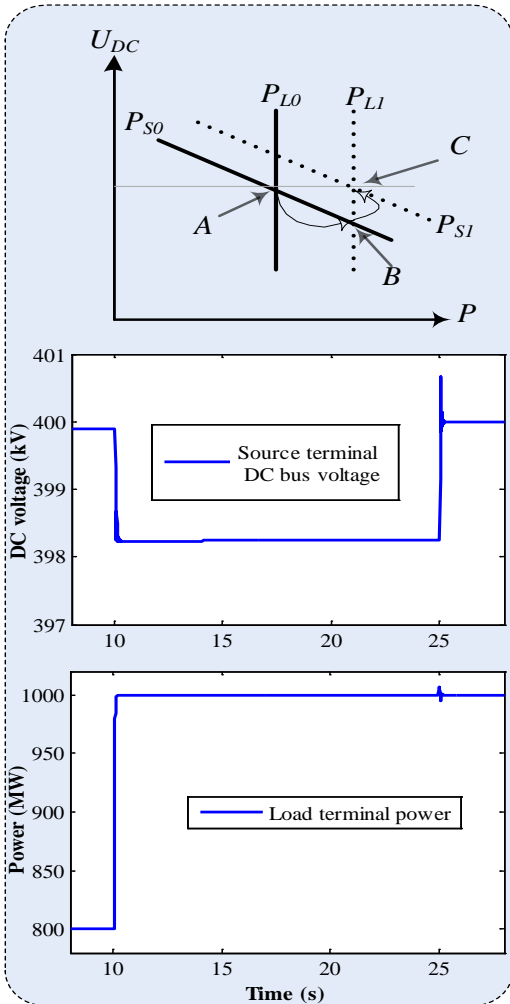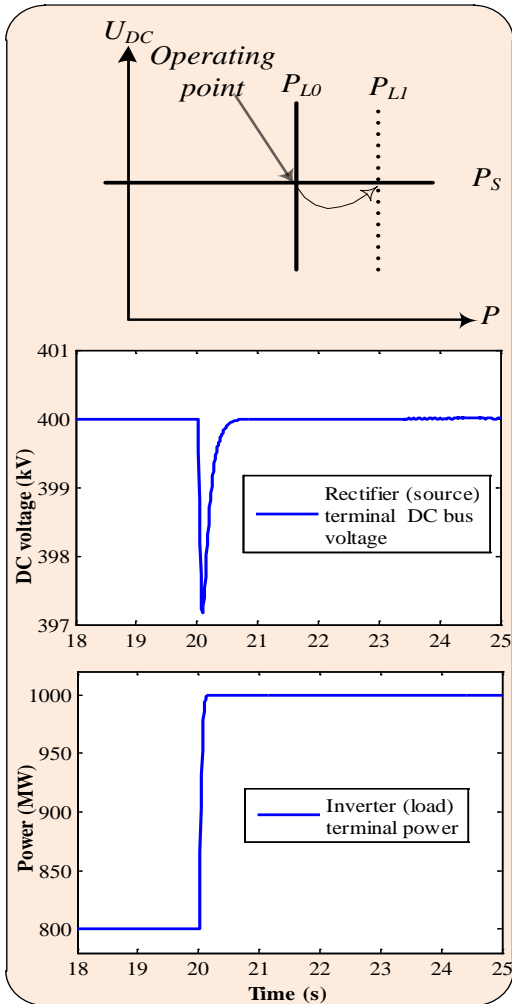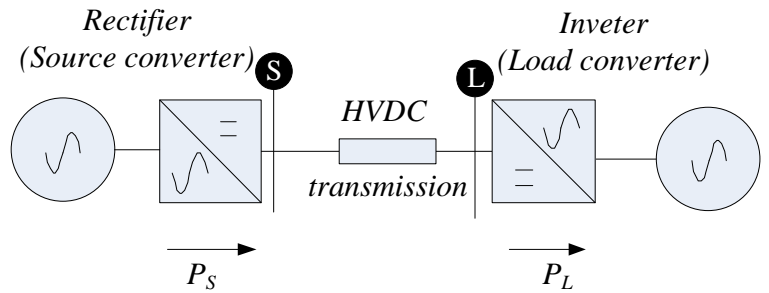

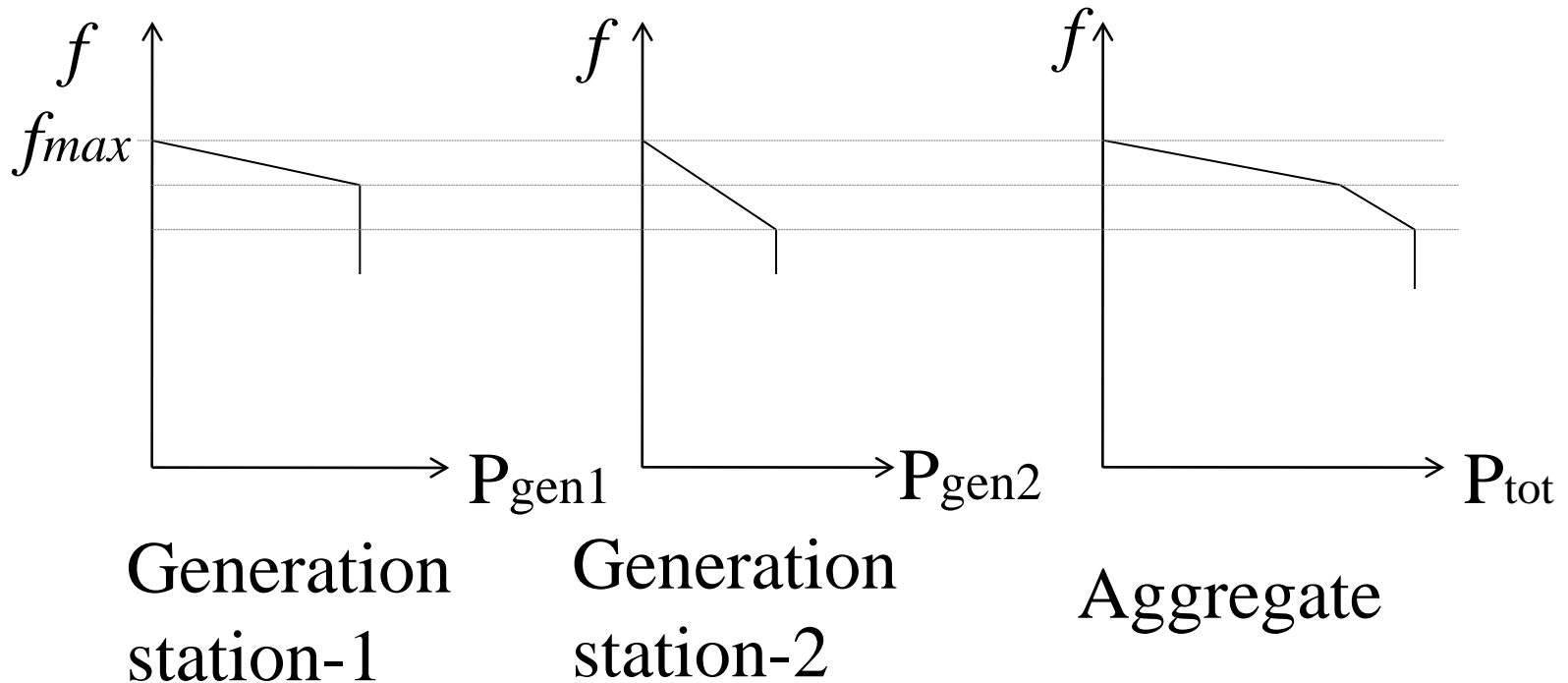Power balance control in AC grids: Traditionally by frequency droop (Primary frequency control)




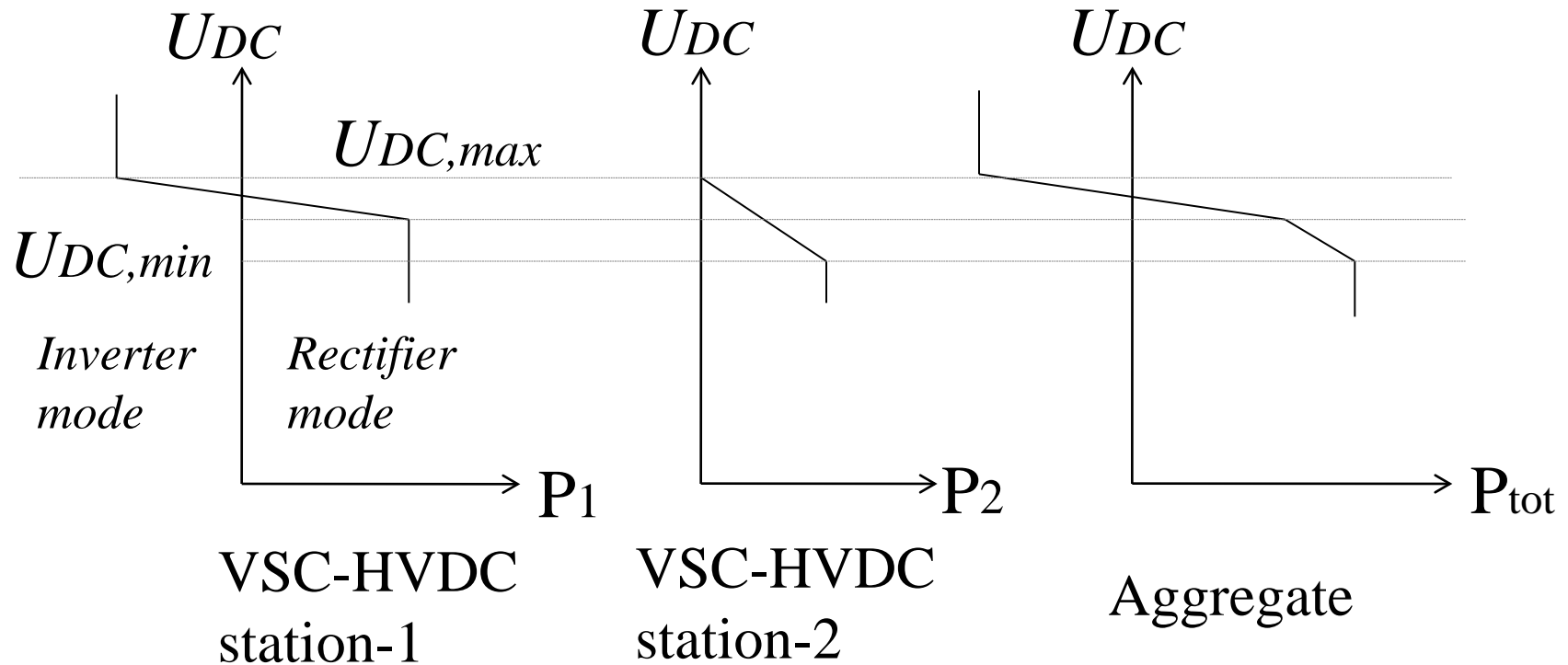Power flow control in DC grid : achieved by DC voltage droop




- No need for communication between terminals
- Many converter terminals contribute to dc voltage regulation
- DC analogy to distributed *frequency droop control* in AC systems





North Sea DC grid: A test model

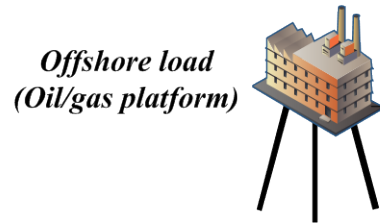

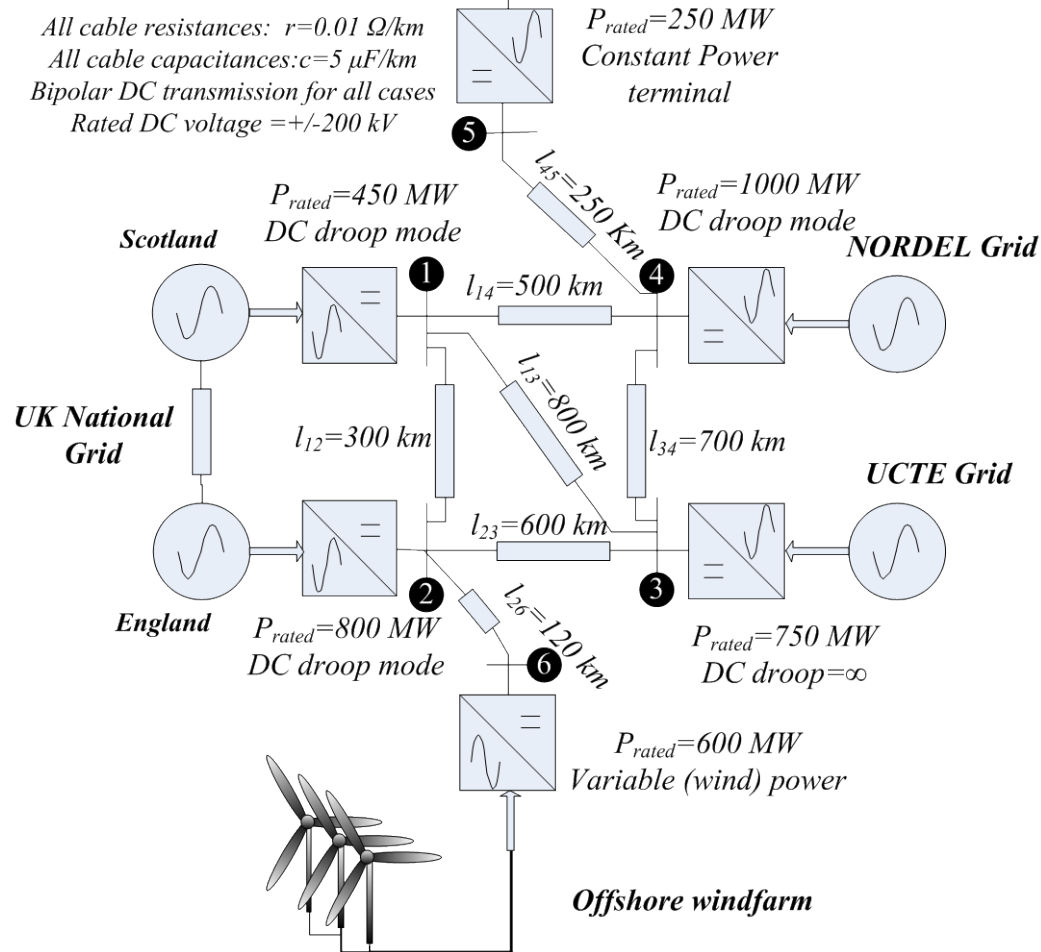All cable resistances: $r=0.01 \Omega/\text{km}$
 All cable capacitances: $c=5 \mu\text{F}/\text{km}$
 Bipolar DC transmission for all cases
 Rated DC voltage = $\pm 200 \text{ kV}$







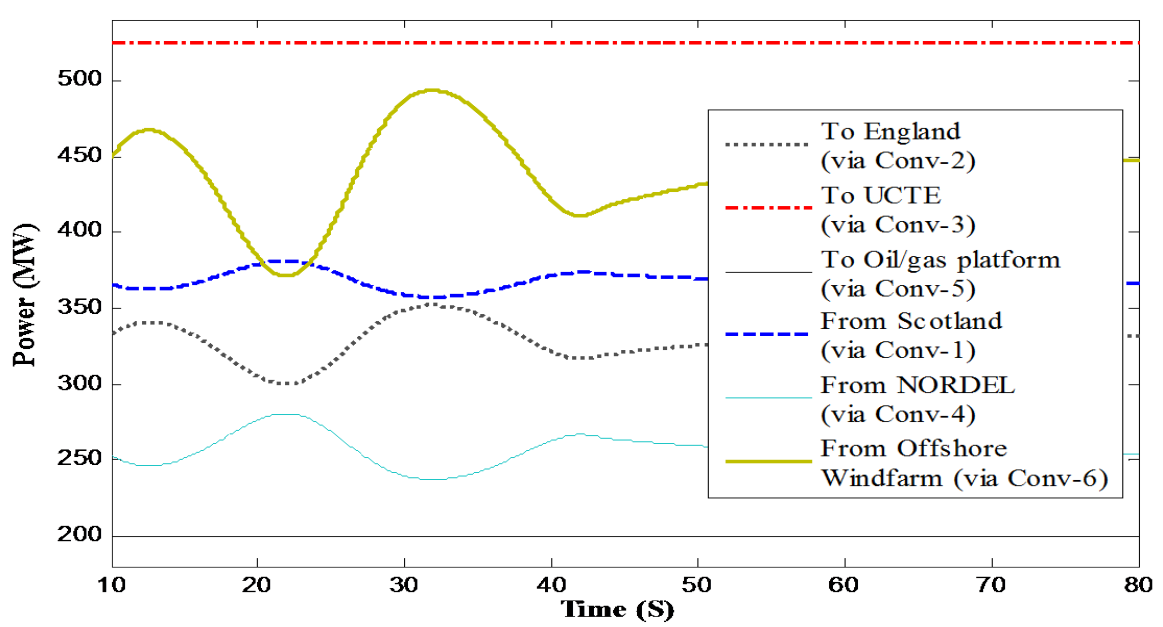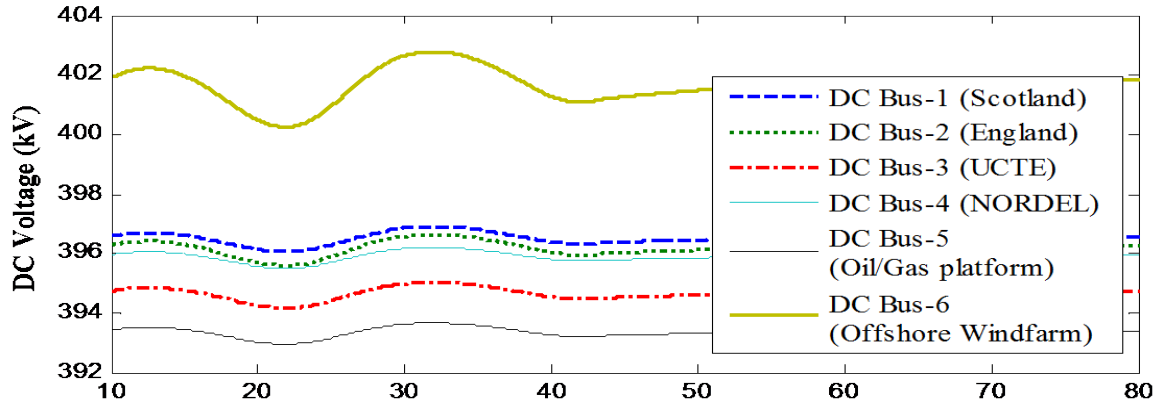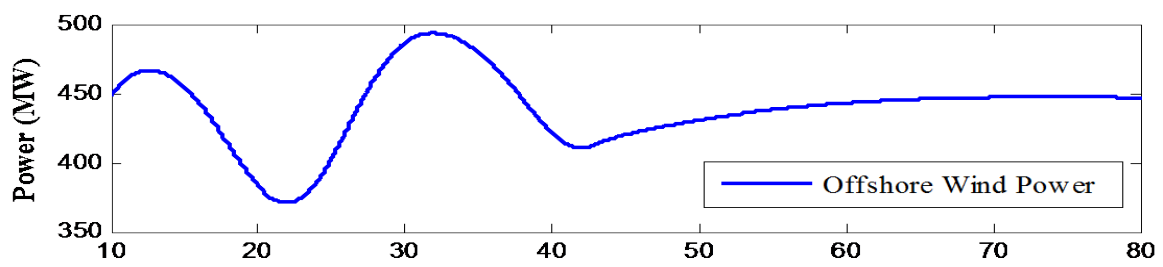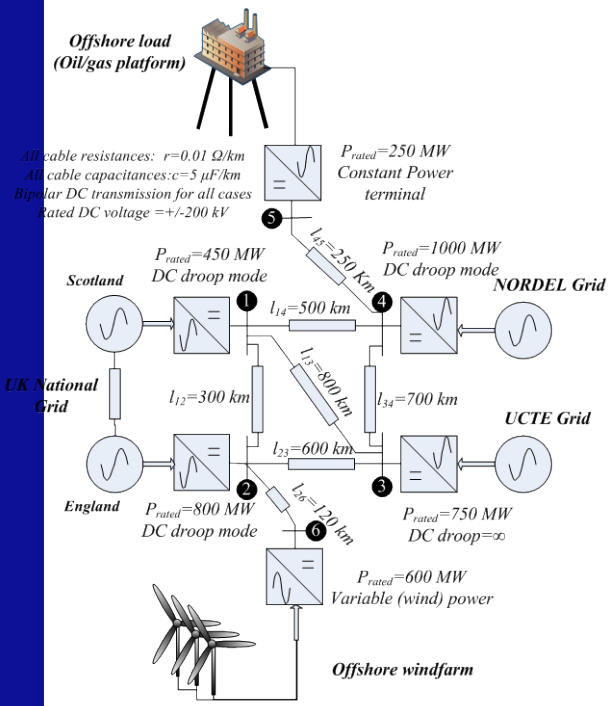Variations of DC voltage with fluctuating wind power and DC droop control responses





Outage of DC line 1-2

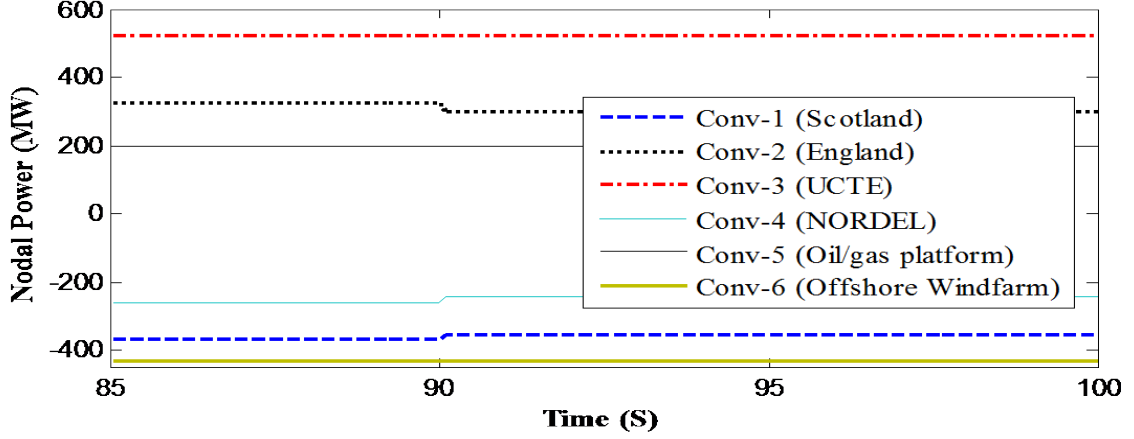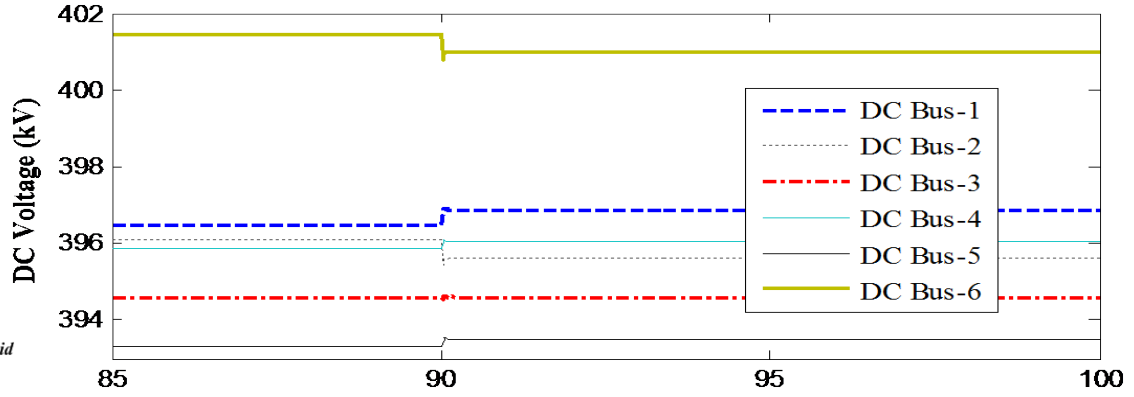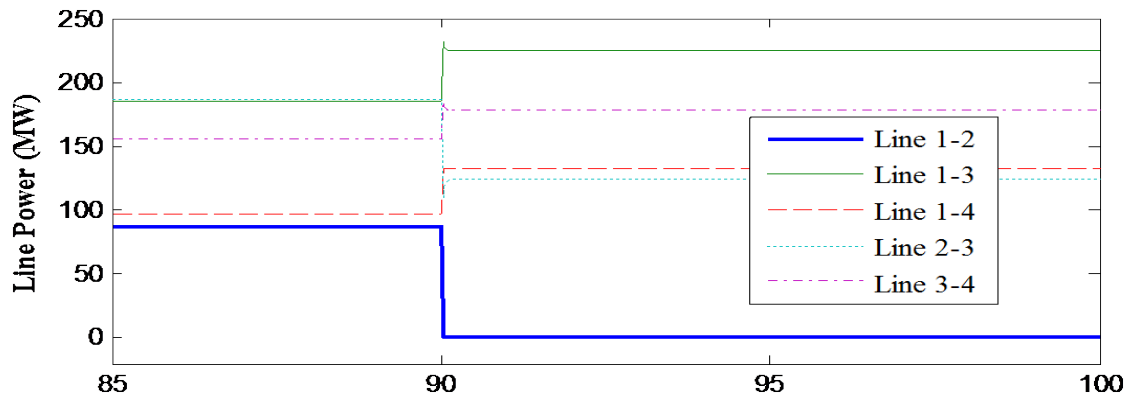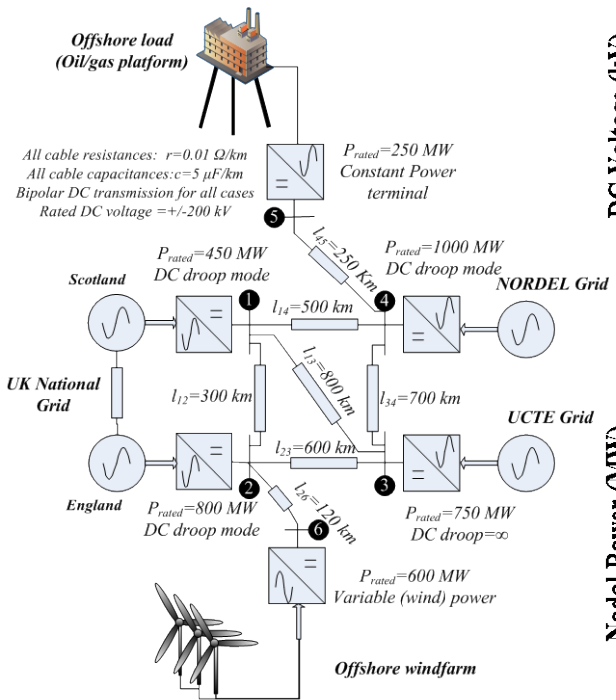Terminal-1 (Conv-1) continues to draw power from DC grid via lines 1-3 and 1-4 when line 1-2 is disconnected.








Outage of connection to windfarm

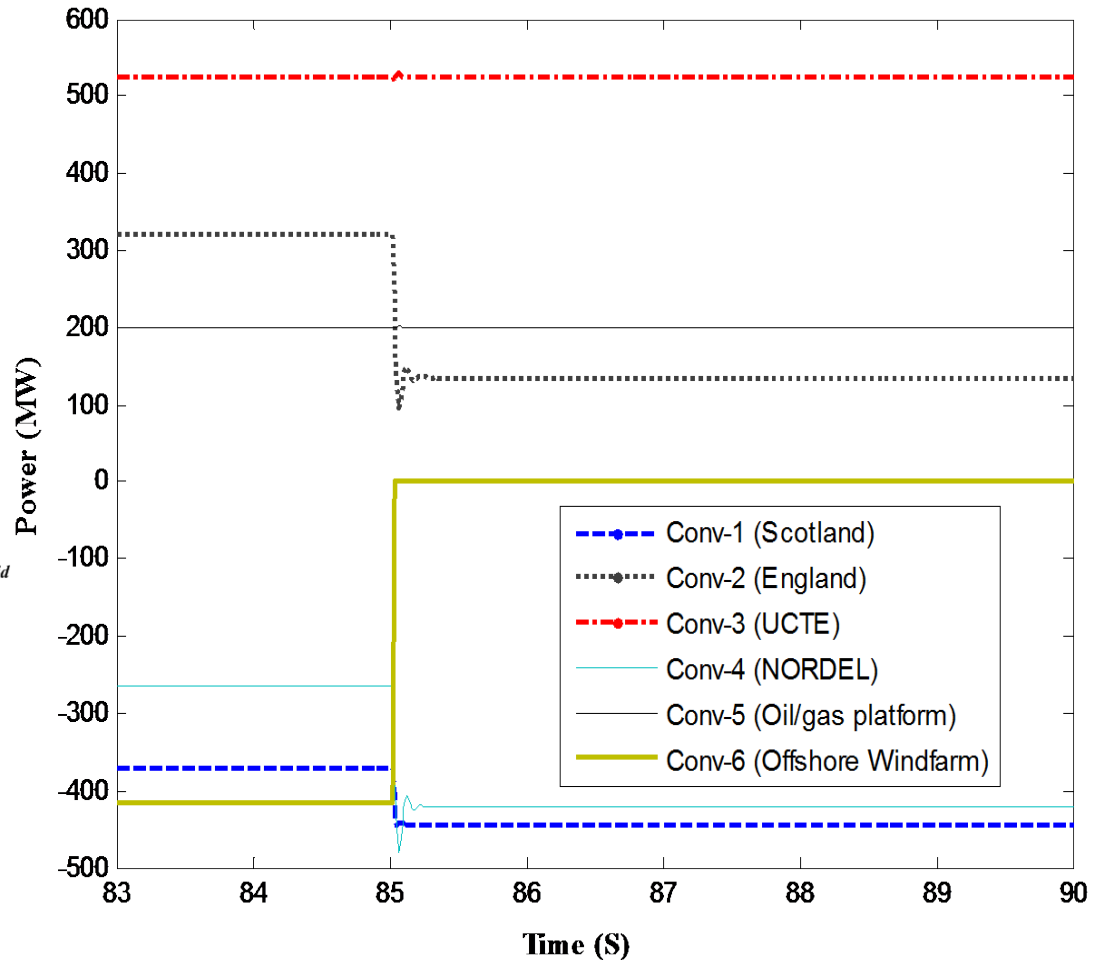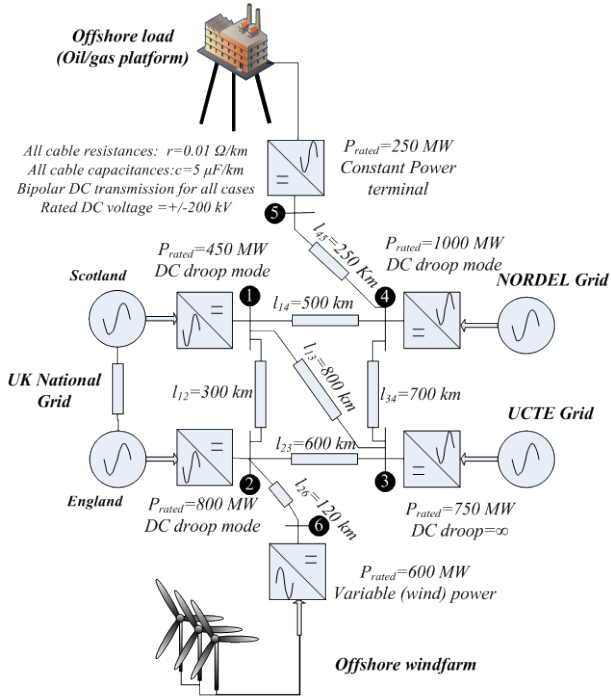


Terminals 1, 2 and 4 compensate for lost power flow from offshore wind farm.

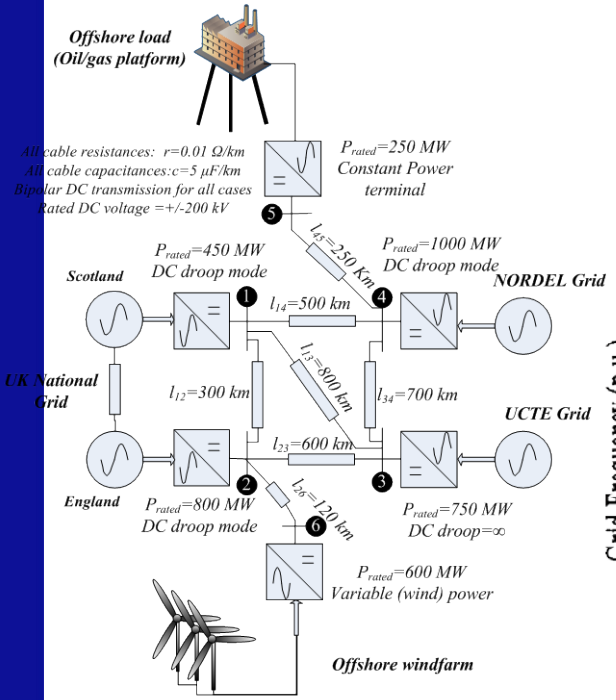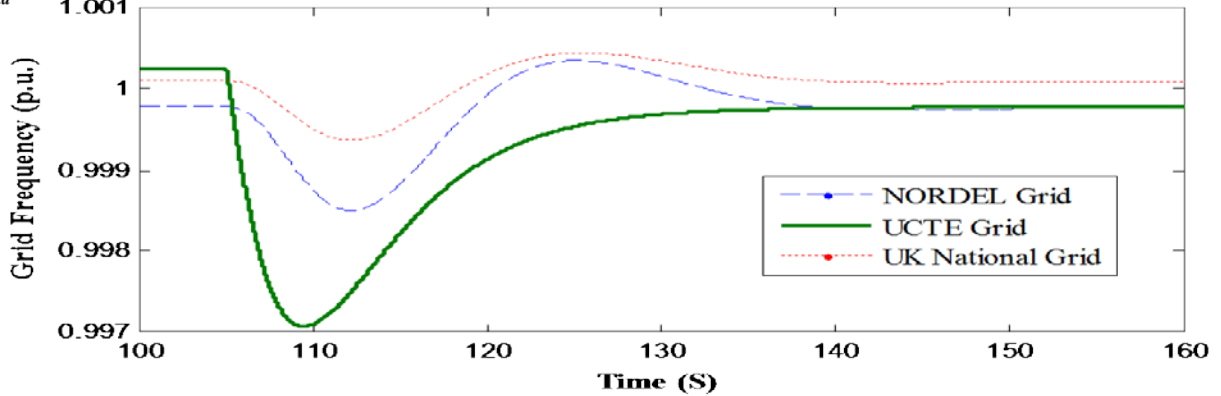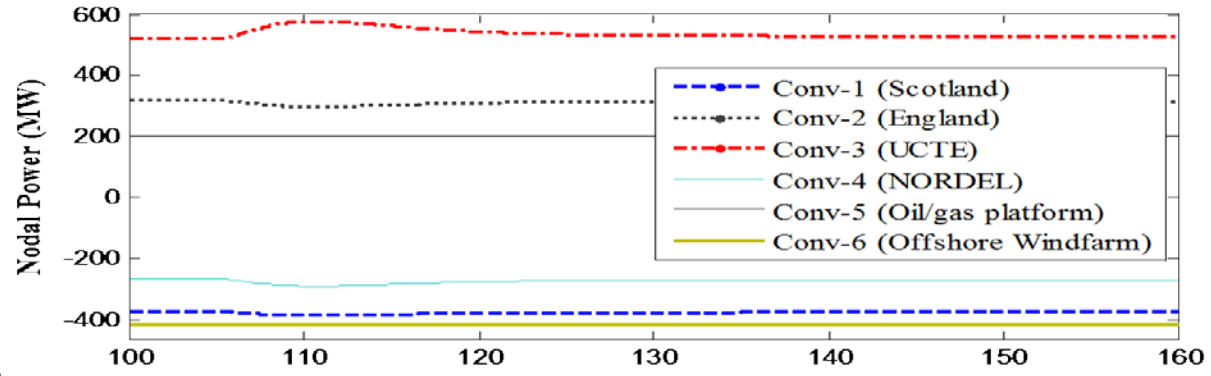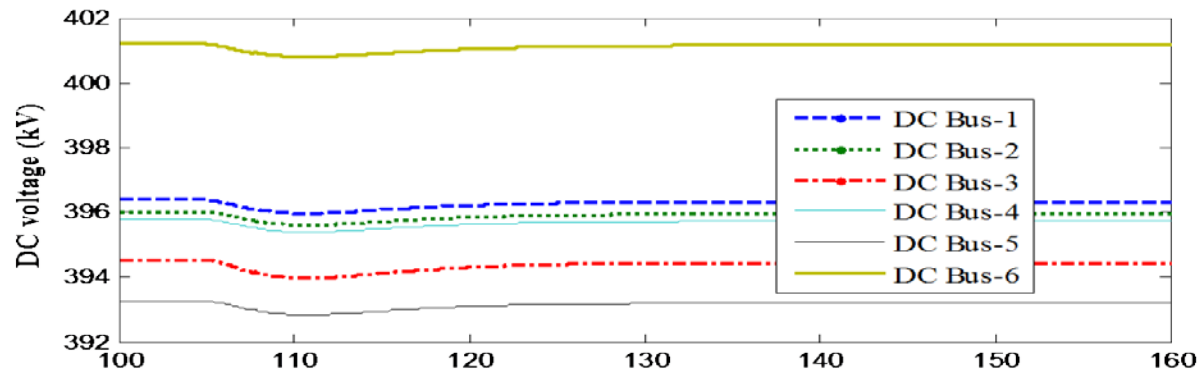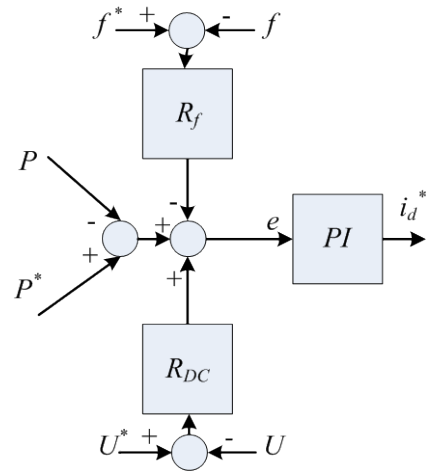Frequency response enhancement of AC grids by MTDC



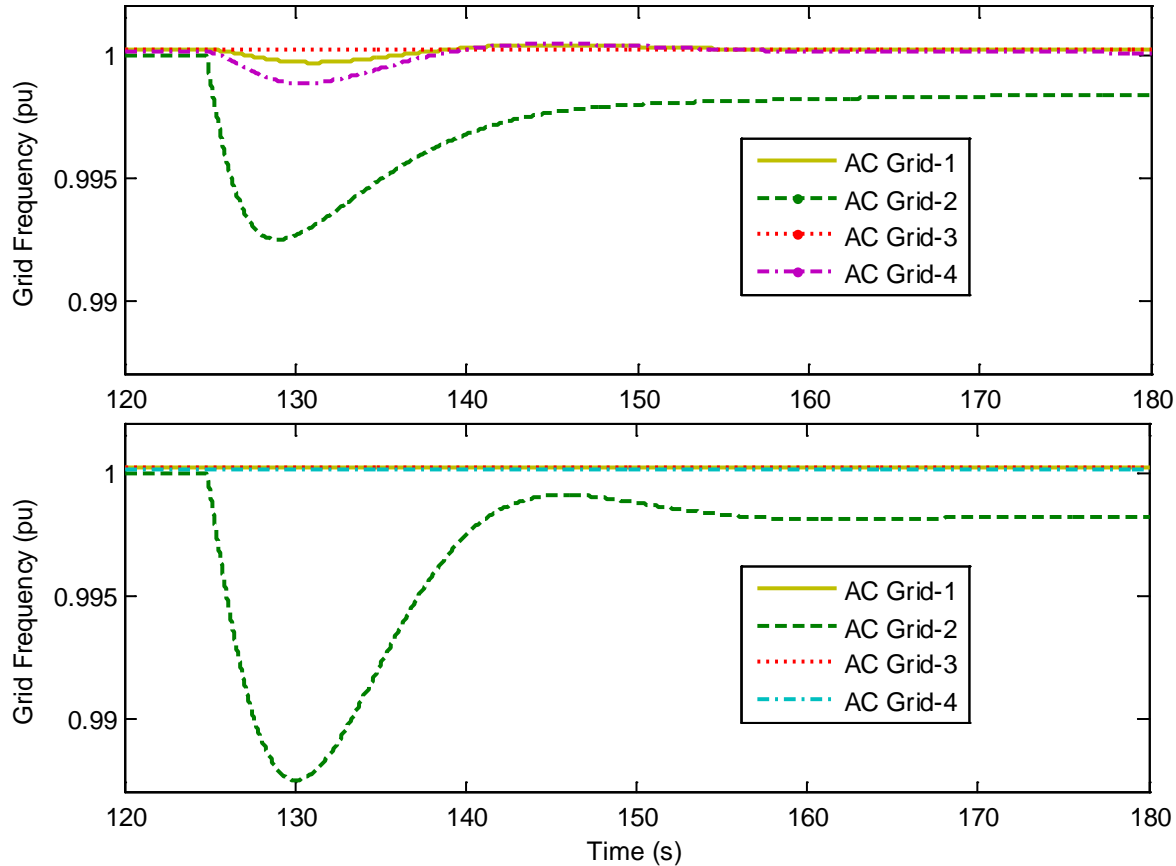Comparison of grid responses: with and without frequency support from DC grid




Frequency response improves with presence of frequency support from DC grid.

Precise control of power flow

Schedule/ dispatch			Control type
Terminal No.	P_{DC} (MW)	U_{DC} (kV)	
1	600	-	Droop
2	-	400	Droop
3	-750	-	Fixed P
4	550	-	Droop
5	-900	-	Fixed P



Control references			Control type
Terminal No.	P_{DC} (MW)	U_{DC} (kV)	
1	600	400	Droop
2	500	400	Droop
3	-750	400	Fixed P
4	550	400	Droop
5	-900	400	Fixed P

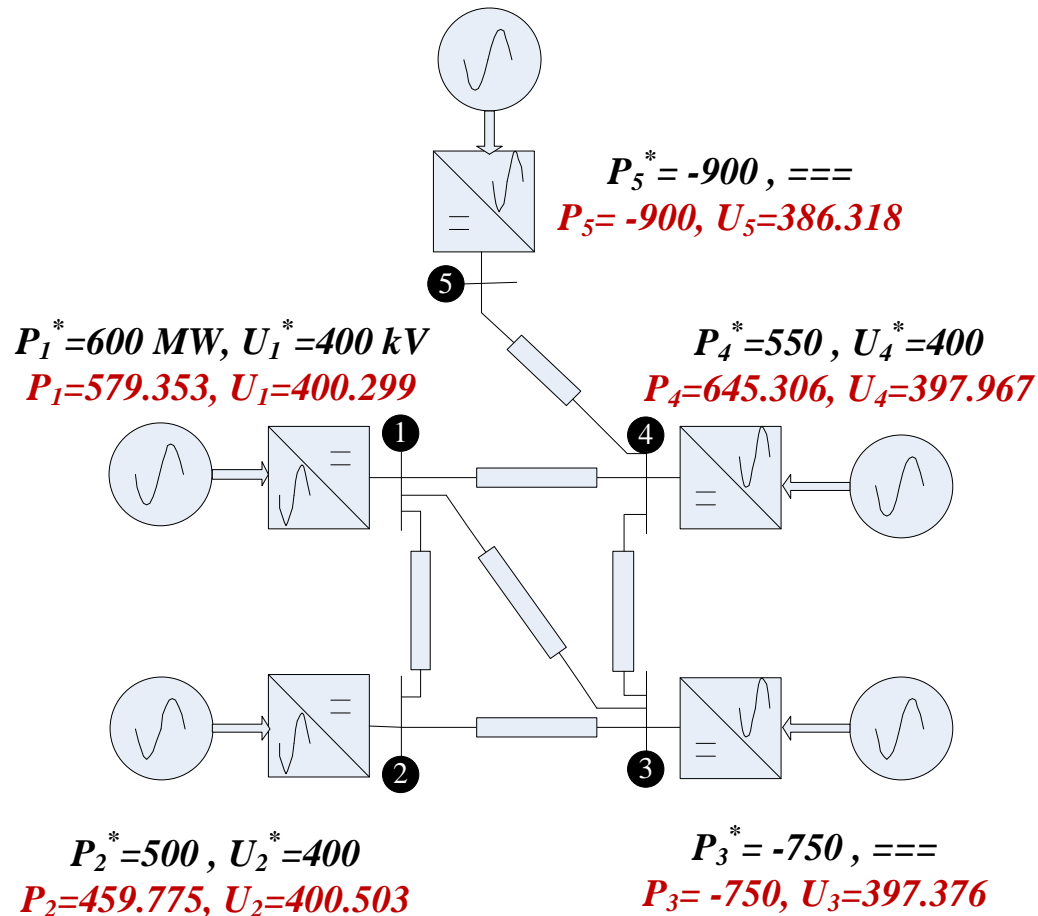


Not precise!

Cntd...

Schedule/ dispatch			Control type
Termina I No.	P _{DC} (MW)	U _{DC} (kV)	
1	600	-	Droop
2	-	400	Droop
3	-750	-	Fixed P
4	550	-	Droop
5	-900	-	Fixed P

↓
DC Power flow analysis
 ↓


Control references			Control type
Termina I No.	P _{DC} (MW)	U _{DC} (kV)	
1	600.00	399.550	Droop
2	535.94	400.000	Droop
3	-750.00	396.613	Fixed P
4	550.00	396.928	Droop
5	-900.00	385.247	Fixed P

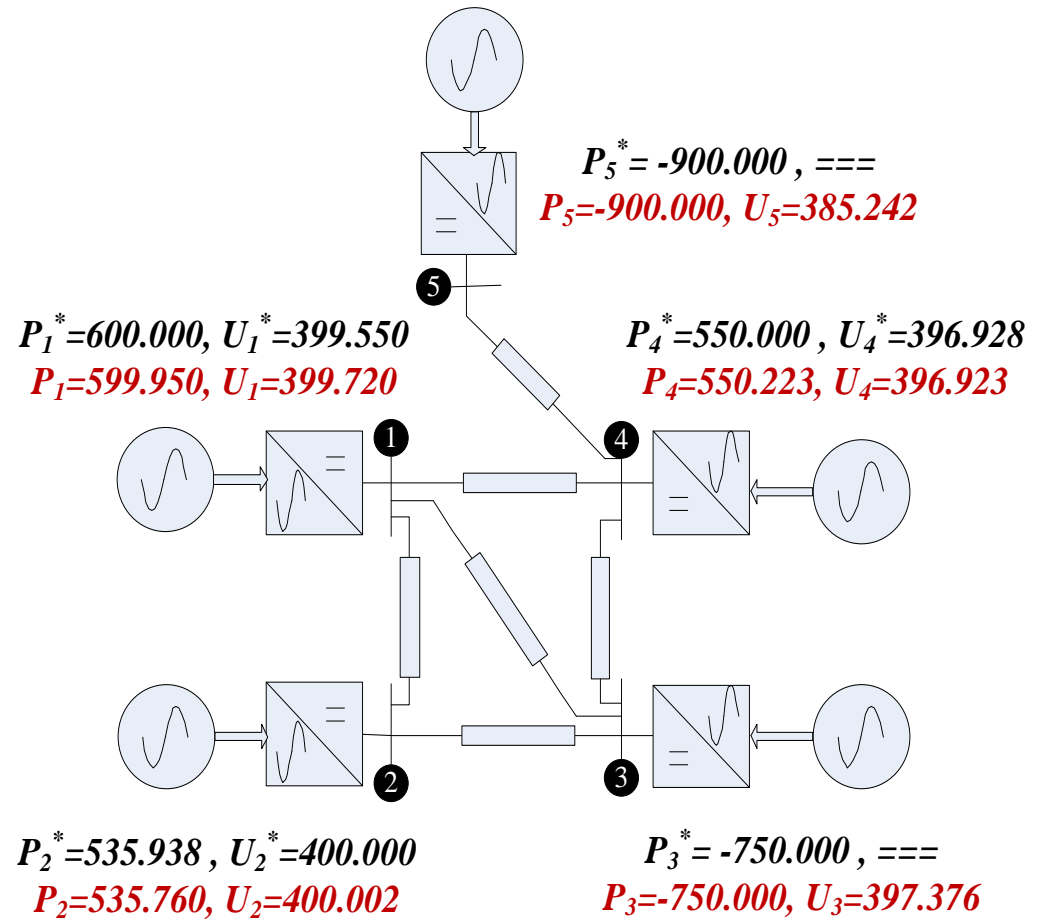

Precise!
 (Desired power flow achieved)

Impact of DC Resistance on DC grid Balancing Power Distribution

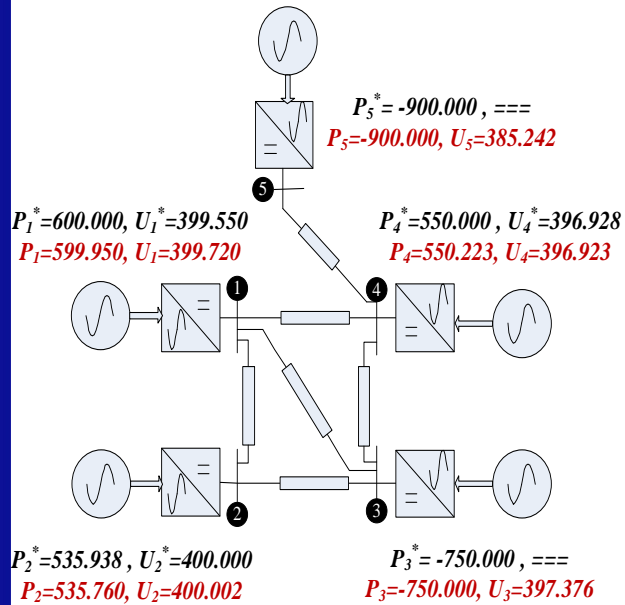- A step change of $\Delta P_3^* = -50$ MW applied to terminal-3
- Unequal compensations, ΔP_{DC} (pu), by terminals-1, 2, 4 & 5 observed



Terminal No.	1	2	3	4	5
U_{DC} (kV)	399.287	399.726	396.204	396.677	385.118
P_{DC} (MW)	618.293	552.483	-800.000	565.853	-900.028
ΔU_{DC} (kV)	-0.263	-0.274	-0.409	-0.251	-0.129
ΔP_{DC} (MW)	14.820	13.723	-50.000	11.741	9.67
P_{Rated} (MW)	900	800	1000	750	1200
ΔP_{DC} (pu)	0.01647	0.01715	-0.05	0.01565	0.00806



Small signal equivalent circuit for studying balancing power distribution

$$R_{o-i} = \frac{\Delta U_{DC-i}}{\Delta I_{DC-i}} = \frac{\Delta U_{DC-i}}{\Delta P_{DC-i} / U_{DC-i}}$$

$$= U_{DC} \frac{U_{Rated-i}}{P_{Rated-i}} \left(\frac{\Delta U_{DC-i} / U_{rated}}{\Delta P_{DC-i} / P_{rated}} \right)$$

$$\approx \rho_{DC-i} \frac{U_{Rated-i}^2}{P_{Rated-i}}$$

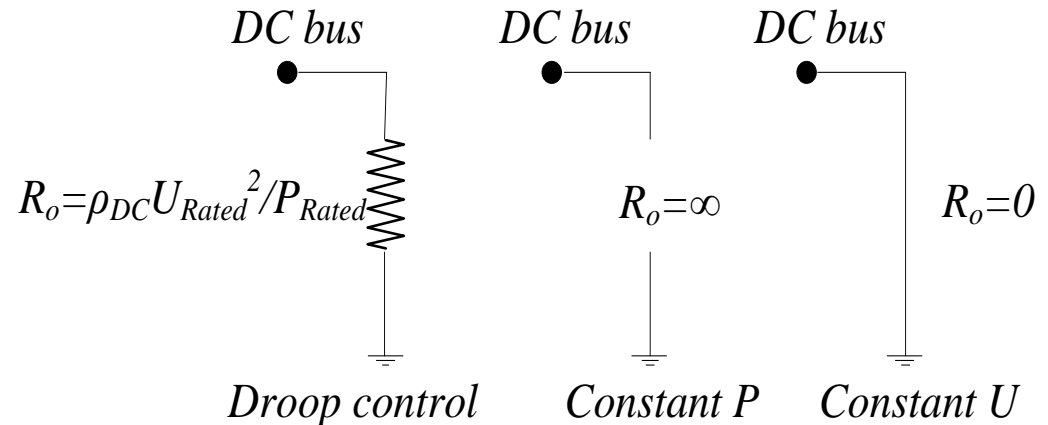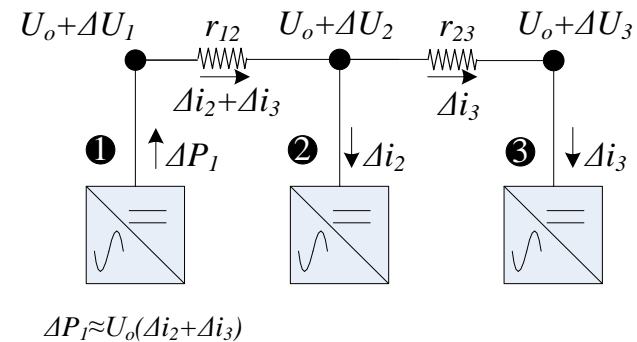
Dynamic output resistance of a VSC station



Example: Small signal circuit for the five terminal VSC-HVDC



Impedances (Ω)	Changes due to $\Delta P_{DC-3}^{ref} = -50$ MW	
	ΔU_{DC} (kV)	ΔP_{DC} (pu)
$Z_{33} = 3.246$	-0.409	-0.05
$Z_{32} = 2.195$	-0.274	0.01715
$Z_{31} = 2.109$	-0.263	0.01647
$Z_{34} = 2.005$	-0.251	0.01565
$Z_{35} = 1.035$	-0.129	0.00806

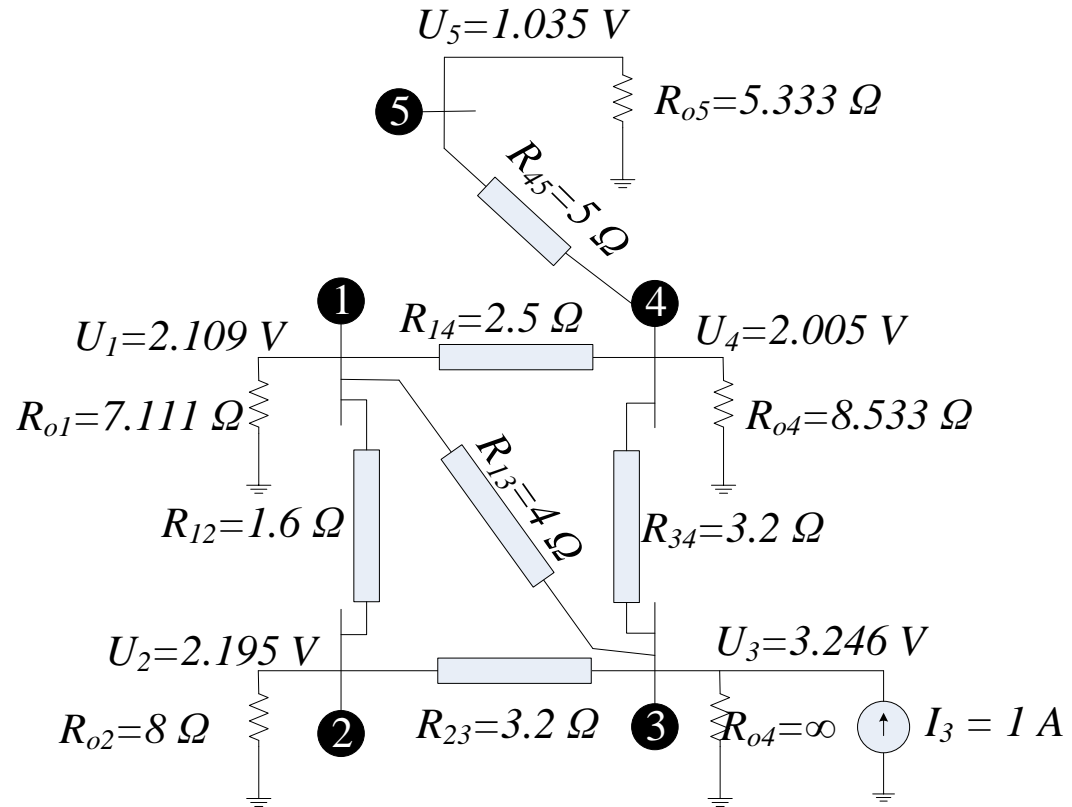Strong droop response for power flow change occurring at closer electrical distance



$$R_{o-i} = \frac{\Delta U_{DC-i}}{\Delta I_{DC-i}} \approx \rho_{DC-i} \frac{U_{Rated-i}^2}{P_{Rated-i}}$$

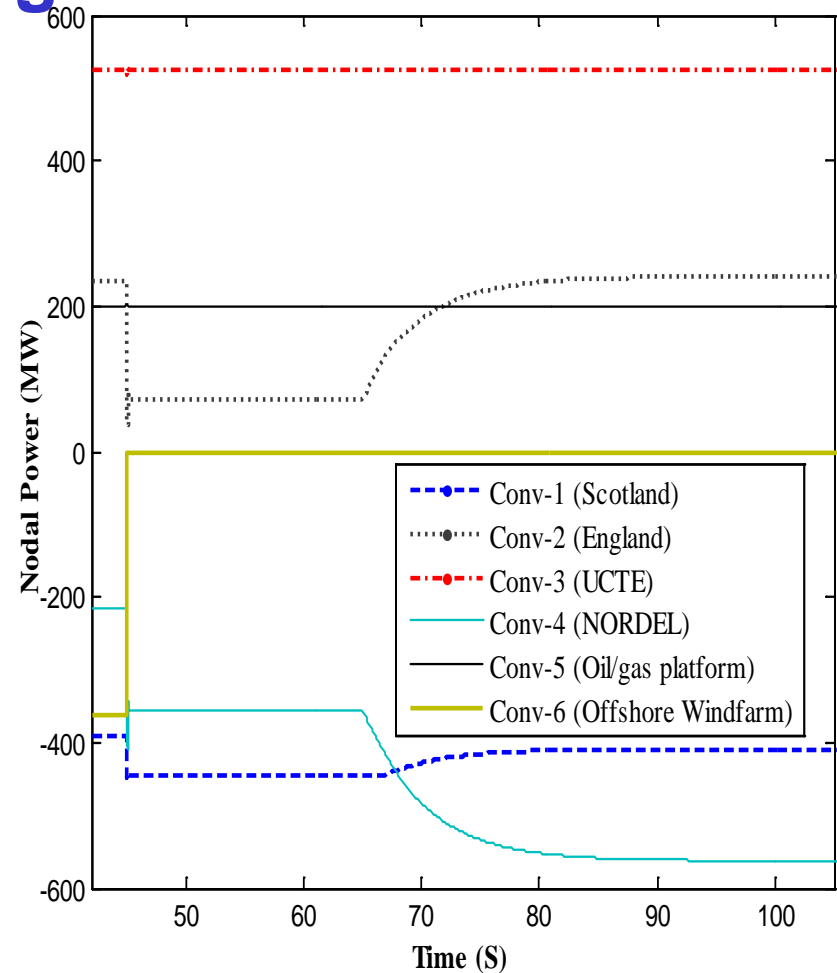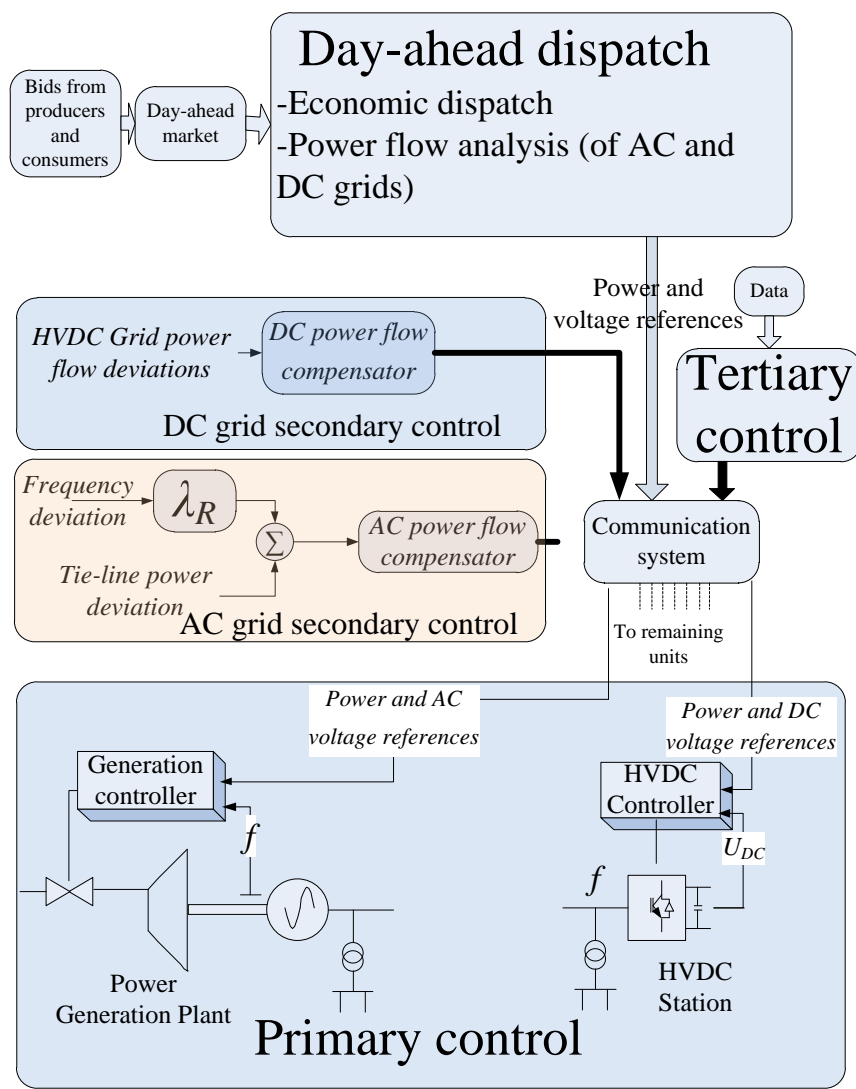Primary, secondary and tertiary controls of AC/DC grids



Secondary control response of HVDC grid for loss of connection to offshore wind farm

Thank you!